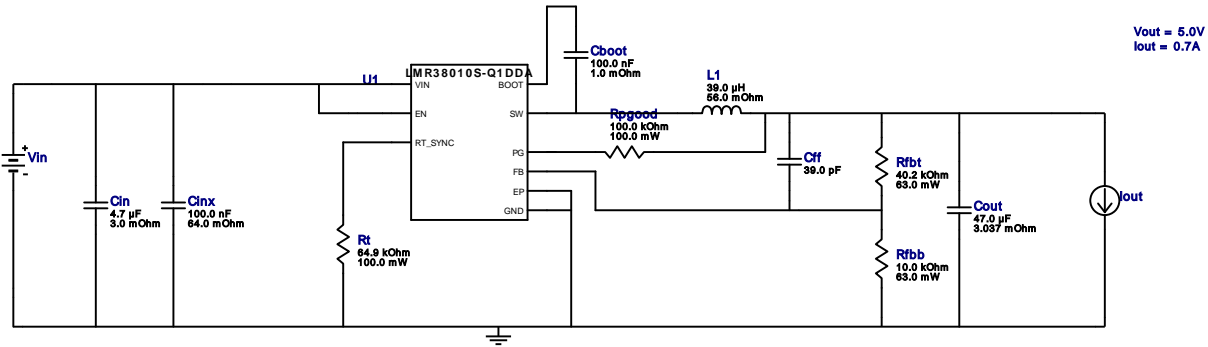


VinMin = 7.0V
VinMax = 36.0V
Vout = 5.0V
Iout = 0.7A

Device = LMR38010SQDDARQ1
Topology = Buck
Created = 2023-07-27 12:31:18.918
BOM Cost = \$3.16
BOM Count = 11
Total Pd = 0.54W

WEBENCH® Design Report

Design : 17 LMR38010SQDDARQ1
LMR38010SQDDARQ1 7V-36V to 5.00V @ 0.7A



Design Alerts







Component Selection Information







The LMR38010S-Q1 is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application. This device support spread spectrum feature which is not modeled on WEBENCH. This device can work in steady state at Vin = 4.2V. However, needs a minimum of 4.5V during start up. See datasheet for details.







Electrical BOM


| Name | Manufacturer | Part Number | Properties | Qty | Price | Footprint |
|-------|------------------|---|---|-----|--------|--------------------------------|
| Cboot | MuRata | GRM155R71C104KA88D Series= X7R | Cap= 100.0 nF ESR= 1.0 mOhm VDC= 16.0 V IRMS= 0.0 A | 1 | \$0.01 | 0402 3 mm ² |
| Cff | TDK | CGA1A2C0G1E390J030BA Series= C0G/NP0 | Cap= 39.0 pF VDC= 25.0 V IRMS= 0.0 A | 1 | \$0.01 | 0201 2 mm ² |
| Cin | MuRata | GRM31CR71H475KA12L Series= X7R | Cap= 4.7 uF ESR= 3.0 mOhm VDC= 50.0 V IRMS= 4.98 A | 1 | \$0.10 | 1206 11 mm ² |
| Cinx | Kemet | C0805C104M5RACTU Series= X7R | Cap= 100.0 nF ESR= 64.0 mOhm VDC= 50.0 V IRMS= 1.64 A | 1 | \$0.01 | 0805 7 mm ² |
| Cout | MuRata | GRM32ER61C476KE15L Series= X5R | Cap= 47.0 uF ESR= 3.037 mOhm VDC= 16.0 V IRMS= 4.59346 A | 1 | \$0.17 | 1210_280 15 mm ² |
| L1 | Würth Elektronik | 7447709390 | L= 39.0 uH 56.0 mOhm | 1 | \$1.48 | WE-PD_1210 196 mm ² |
| Rfbb | Vishay-Dale | CRCW040210K0FKED Series= CRCW...e3 | Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0% | 1 | \$0.01 | 0402 3 mm ² |
| Rfbb | Vishay-Dale | CRCW040240K2FKED Series= CRCW...e3 | Res= 40.2 kOhm Power= 63.0 mW Tolerance= 1.0% | 1 | \$0.01 | 0402 3 mm ² |

| Name | Manufacturer | Part Number | Properties | Qty | Price | Footprint |
|--------|-------------------|--------------------------------------|---|-----|--------|-------------------------------|
| Rpgood | Vishay-Dale | CRCW0603100KFKEA Series= CRCW..e3 | Res= 100.0 kOhm Power= 100.0 mW Tolerance= 1.0% | 1 | \$0.01 | 0603 5 mm ² |
| Rt | Vishay-Dale | CRCW060364K9FKEA Series= CRCW..e3 | Res= 64.9 kOhm Power= 100.0 mW Tolerance= 1.0% | 1 | \$0.01 | 0603 5 mm ² |
| U1 | Texas Instruments | LMR38010SQDDARQ1 | Switcher | 1 | \$1.34 | DDA0008E_N 55 mm ² |

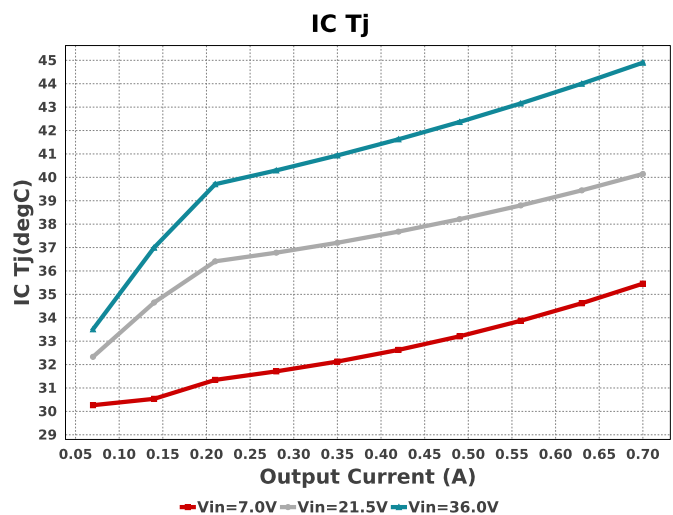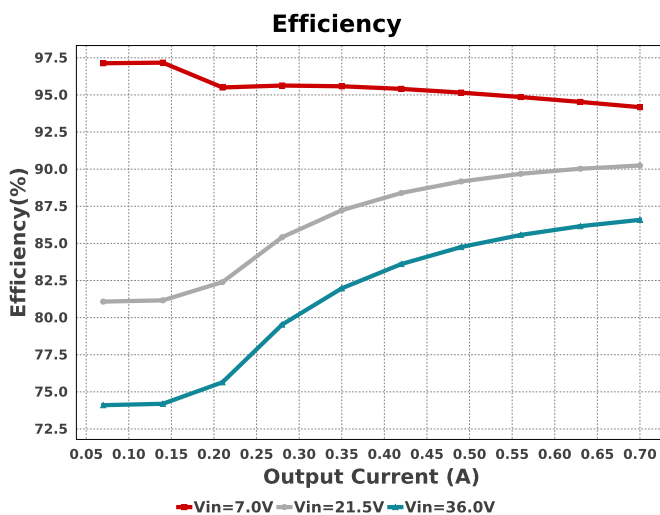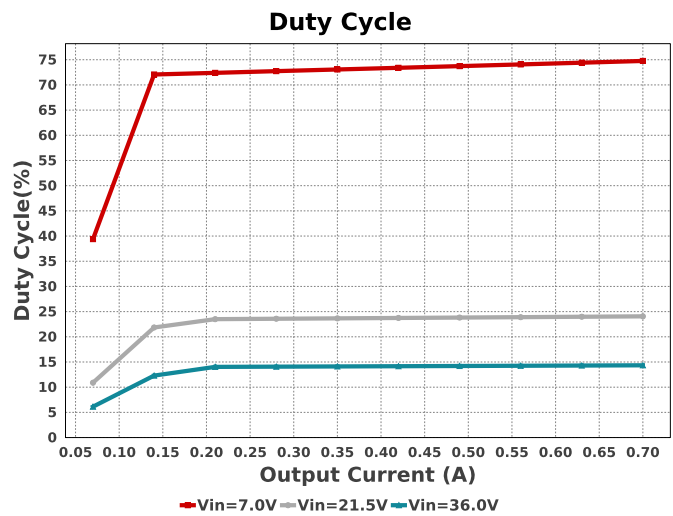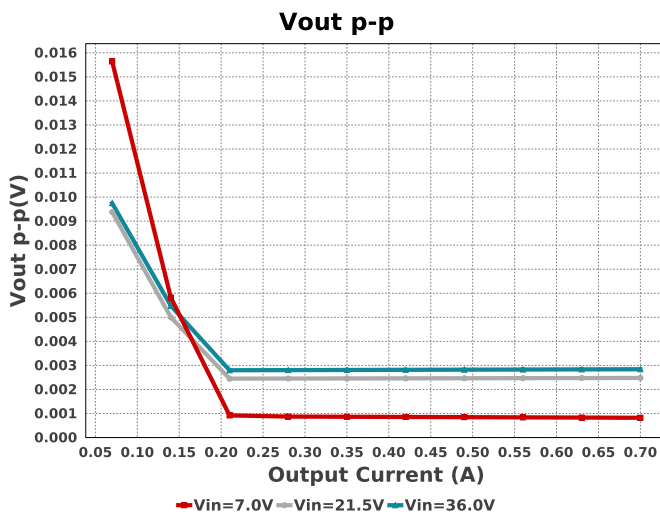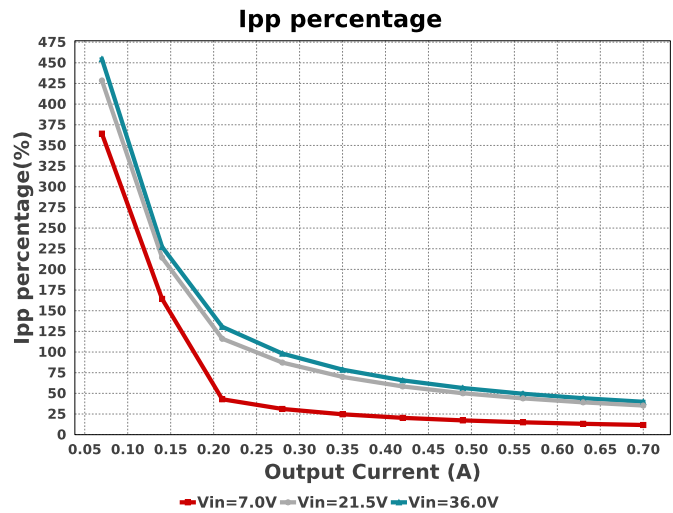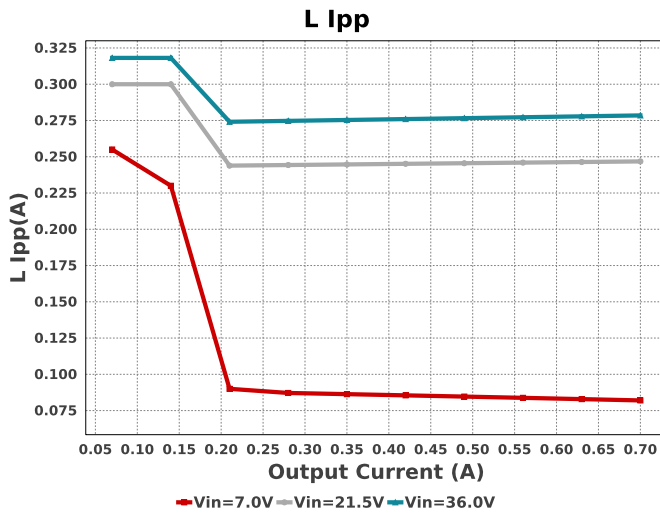DDA0008E_N 55 mm²

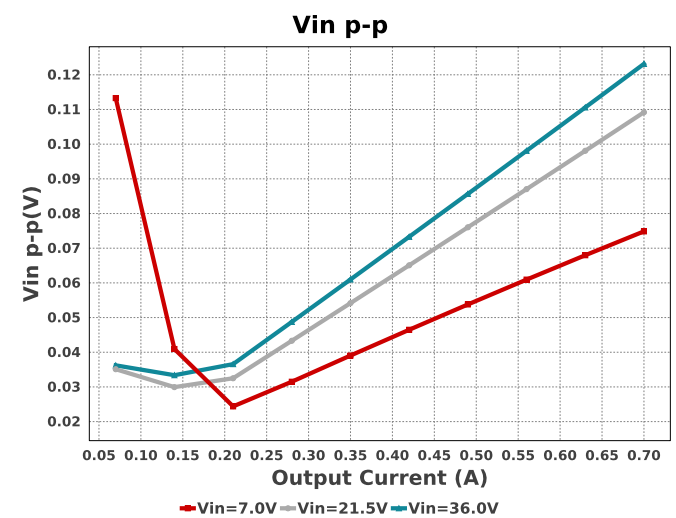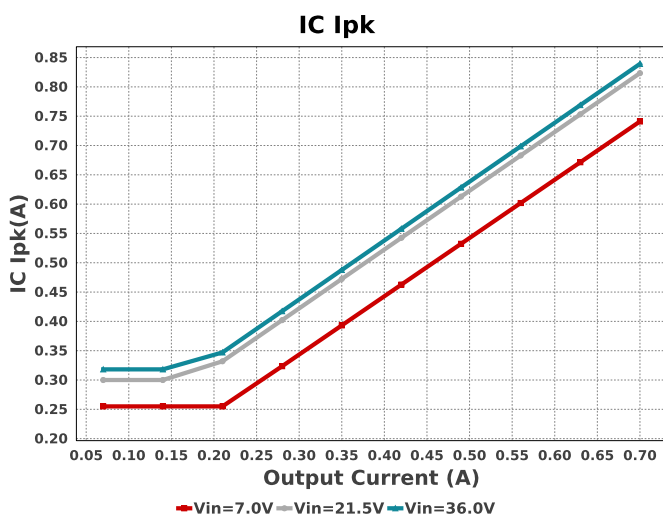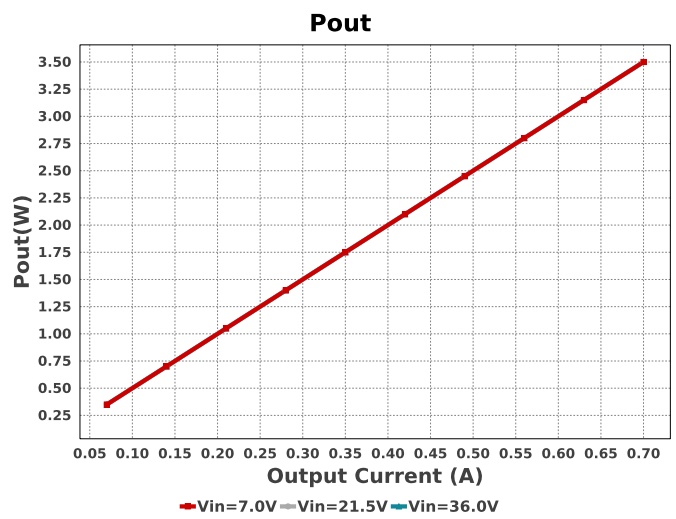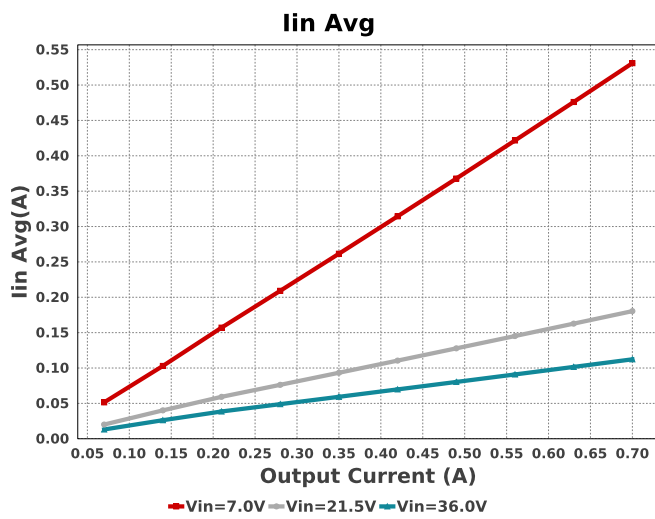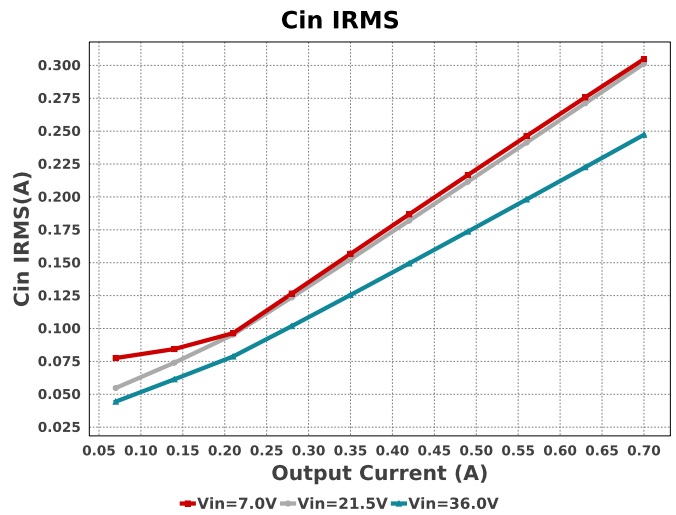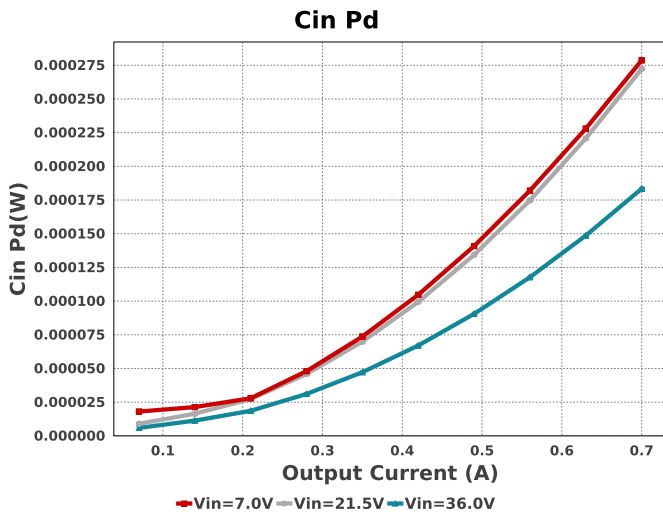

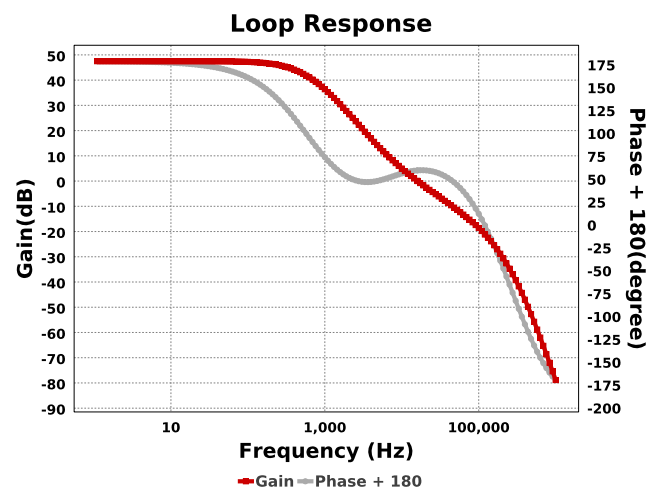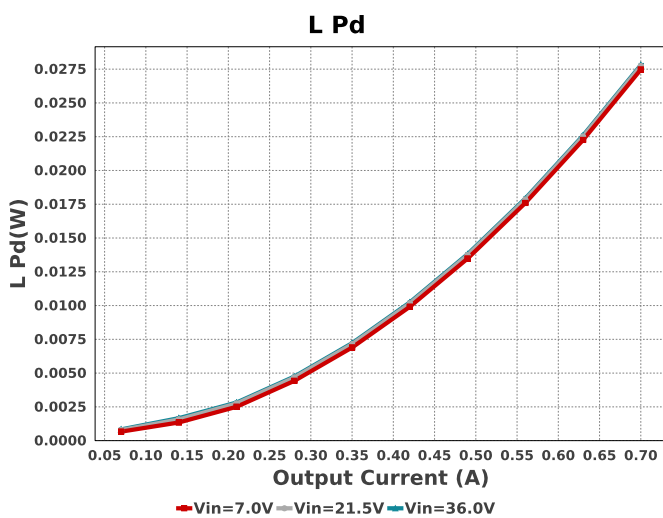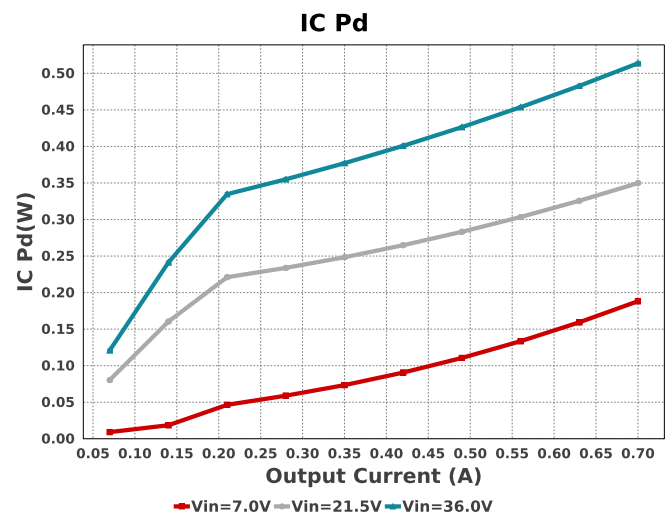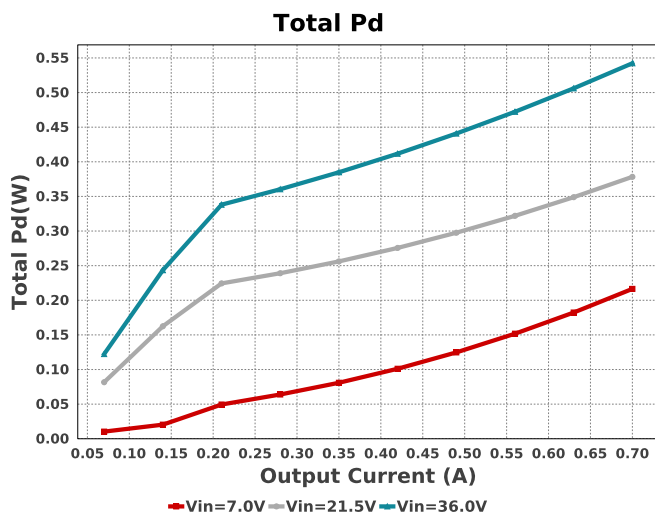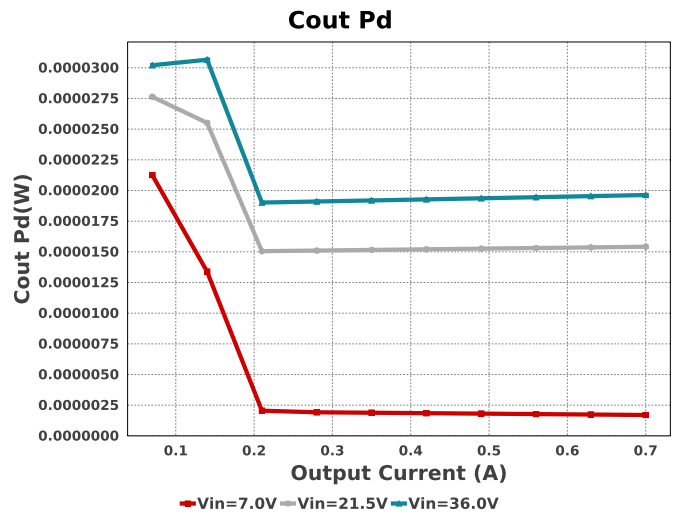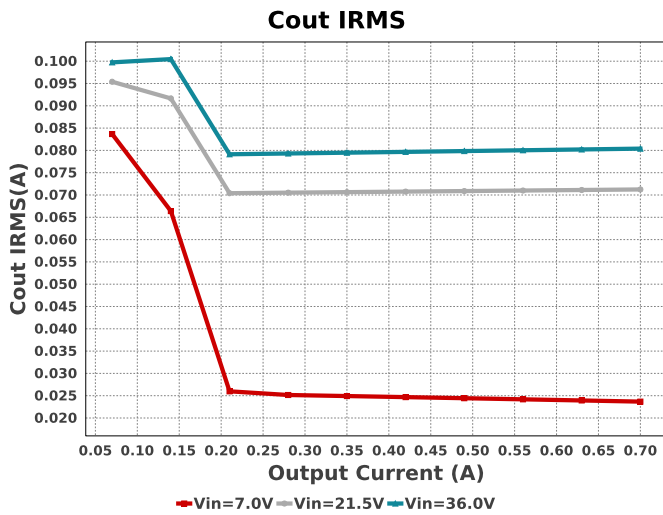

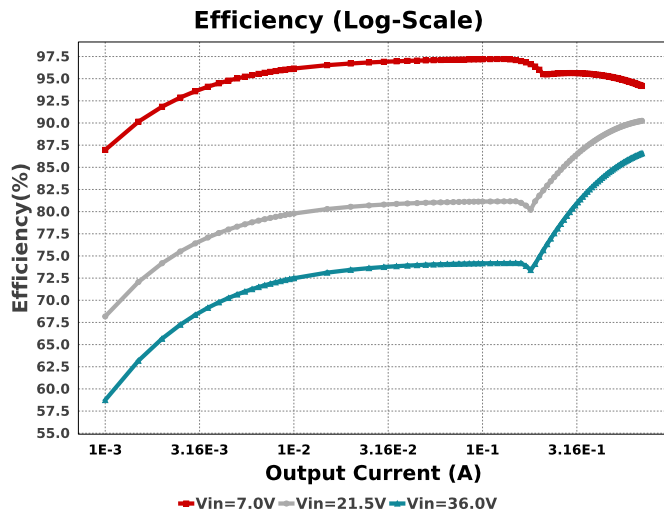

Operating Values

| # | Name | Value | Category | Description |
|-----|---|-----------------------|--------------------|--|
| 1. | Cin IRMS | 247.249 mA | Capacitor | Input capacitor RMS ripple current |
| 2. | Cin Pd | 183.4 μ W | Capacitor | Input capacitor power dissipation |
| 3. | Cout IRMS | 80.395 mA | Capacitor | Output capacitor RMS ripple current |
| 4. | Cout Pd | 19.629 μ W | Capacitor | Output capacitor power dissipation |
| 5. | IC Ipk | 839.249 mA | IC | Peak switch current in IC |
| 6. | IC Pd | 513.77 mW | IC | IC power dissipation |
| 7. | IC Tj | 44.899 degC | IC | IC junction temperature |
| 8. | IC Tolerance | 5.0 mV | IC | IC Feedback Tolerance |
| 9. | ICThetaJA Effective | 29.0 degC/W | IC | Effective IC Junction-to-Ambient Thermal Resistance |
| 10. | Iin Avg | 112.29 mA | IC | Average input current |
| 11. | Ipp percentage | 39.785 % | Inductor | Inductor ripple current percentage (with respect to average inductor current) |
| 12. | L Ipp | 278.498 mA | Inductor | Peak-to-peak inductor ripple current |
| 13. | L Pd | 27.802 mW | Inductor | Inductor power dissipation |
| 14. | Cin Pd | 183.4 μ W | Power | Input capacitor power dissipation |
| 15. | Cout Pd | 19.629 μ W | Power | Output capacitor power dissipation |
| 16. | IC Pd | 513.77 mW | Power | IC power dissipation |
| 17. | L Pd | 27.802 mW | Power | Inductor power dissipation |
| 18. | Total Pd | 542.293 mW | Power | Total Power Dissipation |
| 19. | BOM Count | 11 | System | Total Design BOM count |
| 20. | Cross Freq | 16.035 kHz | System Information | Bode plot crossover frequency |
| 21. | Duty Cycle | 14.344 % | System Information | Duty cycle |
| 22. | Efficiency | 86.585 % | System Information | Steady state efficiency |
| 23. | FootPrint | 304.0 mm ² | System Information | Total Foot Print Area of BOM components |
| 24. | Frequency | 405.78 kHz | System Information | Switching frequency |
| 25. | Gain Marg | -21.139 dB | System Information | Bode Plot Gain Margin |
| 26. | Inductor ripple current requirement used for Inductor selection | 40.0 % | System Information | Custom Inductor ripple current (% of average inductor current) requirement used for Inductor selection |
| 27. | Iout | 700.0 mA | System Information | Iout operating point |
| 28. | Iout transient step used for Cout calculations | 350.0 mA | System Information | Custom Transient current step requirement that was used for Cout selection (A). |
| 29. | Low Freq Gain | 47.498 dB | System Information | Gain at 1Hz |
| 30. | Mode | CCM | System Information | Conduction Mode |
| 31. | Overshoot Value | 15.073 mV | System Information | Theoretical Vout Overshoot Value |
| 32. | Phase Marg | 60.49 deg | System Information | Bode Plot Phase Margin |
| 33. | Pout | 3.5 W | System Information | Total output power |
| 34. | Total BOM | \$3.16 | System Information | Total BOM Cost |

| # | Name | Value | Category | Description |
|-----|---|------------|--------------------|--|
| 35. | Undershoot Value | 25.864 mV | System Information | Theoretical Vout Undershoot Value |
| 36. | Vin | 36.0 V | System Information | Vin operating point |
| 37. | Vin p-p | 123.154 mV | System Information | Peak-to-peak input voltage |
| 38. | Vout | 5.0 V | System Information | Operational Output Voltage |
| 39. | Vout Actual | 5.02 V | System Information | Vout Actual calculated based on selected voltage divider resistors |
| 40. | Vout Ripple requirement used for Cout calculations | 1.0 % | System Information | Custom maximum output ripple requirement that was used for Cout selection(% of Vout). |
| 41. | Vout Tolerance | 2.126 % | System Information | Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable |
| 42. | Vout p-p | 2.841 mV | System Information | Peak-to-peak output ripple voltage |
| 43. | Vout transient requirement used for Cout calculations | 3.0 % | System Information | Custom Transient voltage change requirement that was used for Cout selection (% of Vout). |

Design Inputs

| Name | Value | Description |
|---------|--------------|------------------------|
| Iout | 700.0 m | Maximum Output Current |
| VinMax | 36.0 | Maximum input voltage |
| VinMin | 7.0 | Minimum input voltage |
| Vout | 5.0 | Output Voltage |
| base_pn | LMR38010S-Q1 | Base Product Number |
| source | DC | Input Source Type |
| Ta | 30.0 | Ambient temperature |

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of $L1$ before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board

If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab down to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 7.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum load of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.



Design Assistance

1. Master key : 9BEBB61A34925AAD[v1]
2. **LMR38010S-Q1** Product Folder : <http://www.ti.com/product/LMR38010%2DQ1> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with TI products.